

Clippers & Clampers

Objectives:-

- Sketch each of the following circuits: series clipper, shunt clipper, biased shunt clipper, zener diode clipper, clamping circuit, and biased clamper circuit.
- Draw input & output waveforms for each of the above circuits and explain the circuit operation.
- Design each of the above circuit and select suitable components.
- Analyze each of the above circuits to determine its performance.

Introduction:-

Because it passes a large current when forward biased and an extremely small current when reverse biased, a semiconductor diode can be employed as a switch. The speed with which a diode can be switched is determined by the reverse recovery time of the device. Diodes are widely applied to chip unwanted portions from a waveform, or to clamp the peak of a waveform at a desired dc level. Zener diodes may be used as reference voltage sources in clipping and clamping circuits.

Experiment No.2

CLIPPING CIRCUITS

Aim:- To design various clipping circuits and check their functionality.

Components and Equipments:- Diode, Zener diodes, Resistors, CRO, Function generator, Power supply, BNC cables, Groove board, clips, transistors.

Circuit diagrams:-

(i) **Biased Positive Clipper:-**


 


Fig2.1.1: Biased Positive Clipper

Piecewise linear

Transmission characteristics.

 

DEPT. OF ECE, NITW

PULSE CIRCUITS LAB

(ii) **Biased Negative Clipper:-**


 


Fig2.1.2: Biased Negative Clipper

 

Transfer characteristics

For good clipping, we should have $R_f \ll R \ll R_r$

$$R = \sqrt{(R_f \cdot R_r)}.$$

(iii) **Two Level Clipper:-**


 


Fig2.1.3: Two Level Clipper

Transfer characteristics

 

(iv) **Double ended clipper:-**


 


Fig2.1.4: Double ended clipper using Zener Diodes

 

Transfer characteristics

Transistor Clipper: -


 


Fig2.1.5: Transistor as a clipper

 

Design:- The input V_i is sinusoidal and large enough to carry the transistor both into saturation and below cutoff. The base is biased so that cutin occurs at the voltage V .

In saturation, however, the collector current will remain constant at

$$I_c = (V_{cc} - V_{cesat})/R_c = I_{cs}$$

This limiting occurs when $i_b > I_{cs}/h_{fe}$

Let us take binary Q (2.5V, 1mA).

$$V_{cc} = 5V$$

$$I_c R_c = 5 - 2.5$$

Then $R_c = 2.5k\Omega$.

- 1) When the transistor is in active region $V_o = -h_{fe} R_c V_i / R_i$
- 2) When it is in cutoff region $V_o = V_{cc}$
- 3) When it is in saturation $V_o = V_{cesat}$.

Procedure:-

- Construct a Biased positive clipper circuit as in figure2.1.1 using a 1N4001 or BY127 diode and a 2.2K Ω resistor.
- Apply a $\pm 10V$, 1KHz square wave input & monitor both input & output waveform ON a (dc-coupled) oscilloscope.
- Sketch the input & output waveforms carefully notify the precise output amplitudes with respect to ground level
- Construct a two level clipper circuit using zener diode. Sketch the input & output waveforms. Carefully notify the output amplitude

CLAMPERS

Aim:-To design clamping circuits and observe their outputs.

Components and Equipments:-Capacitor, Resistors, Diode, Function Generator, CRO, RPS and Transistors.

Circuit diagram:-

1) **Negative Clamper**:-



 


Fig2.2.1: Negative Clamper circuit

Input and output wave forms:-

 

Transfer characteristics

 

Procedure:-

- Construct a negative clamping circuit as in figure2.2.1 using the component values determined in design $R1 = 56K\Omega$ & $C1 = 1\mu f$.
- Apply a $\pm 10V$, $1KHz$ square wave input from a source with a resistance of approximately 500Ω and monitor both input & output waveform on a (dc-coupled) oscilloscope.
- Sketch the input & output waveforms carefully noting the precise output amplitudes with respect to ground level.
- Adjust the signal frequency to $100KHz$ and measure the tilt on the output.

(ii) **Positive Clamper:-**


 


Fig2.2.2: Positive Clamping circuit

 


 


Fig2.2.3: Negative Clamper circuit

I/P & O/P Waveforms:-

 

(iv) **Biased Negative Clamper:-**


 


Fig2.2.4: Biased Negative Clamper circuit

I/P & O/P Waveforms:-

 


 


Fig2.2.5: clamping in the input circuit of an amplifier

Voltage Waveforms at Different Nodes:-

 

Analysis:-

- Explain the shape of the output waveforms from each of the clipping circuits.
- Explain the shape of the output waveforms from each of the clamping circuits.
- Calculate the expected output tilt for the clamping circuit in example 1 (class Note Book) when the signal frequency is 100KHz. Compare to the tilt measured in procedure 2-4.

Conclusion:-

In clamping circuit it is observed that an extremity can be set for positive or negative signal excursion. Hence it is also called DC restorer. We can limit a particular voltage up to some voltage level by reference voltage.