

Full-Adder

A full-adder is a logic circuit having 3 inputs A,B and C_I (which is the carry from the previous stage) and 2 outputs (Sum and Carry), which will perform according to table 3. The full-adder can handle three binary digits at a time and can therefore be used to add binary numbers in general.

The simplest way to construct a full adder is to connect two half- adder and an OR gate as shown in Fig 2-4. The full-adder is then the fundamental logic circuit incorporated in digital computers to perform arithmetic functions.


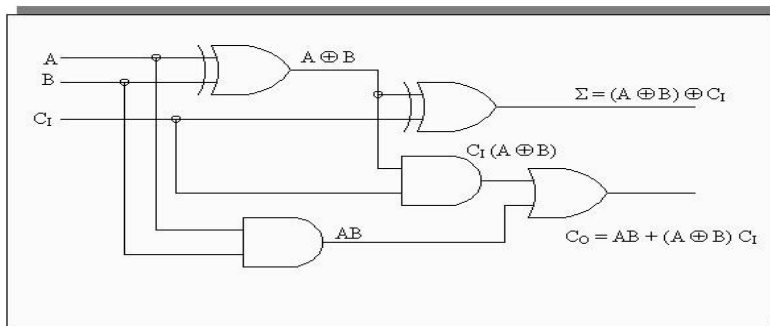


Fig 2.4a

Fig 2.4b

| input | | | output | |
|-------|---|----------------|----------------|---|
| A | B | C _I | C _O | S |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

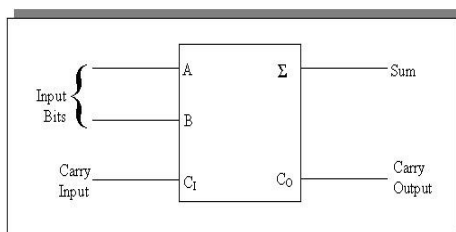

| | | | | |
|--|--|--|--|--|
| | | | | |
|--|--|--|--|--|

Fig 2.4c

Table 3

