


## Experiment No.4

### MONOSTABLE MULTIVIBRATOR

**Aim:-** To design and implement a monostable multivibrator.

**Components and Equipments:-** Transistors, Resistors, Capacitors, CRO, Groove Board, function generator, Diode, DC power supply.

**Circuit Diagram:-**

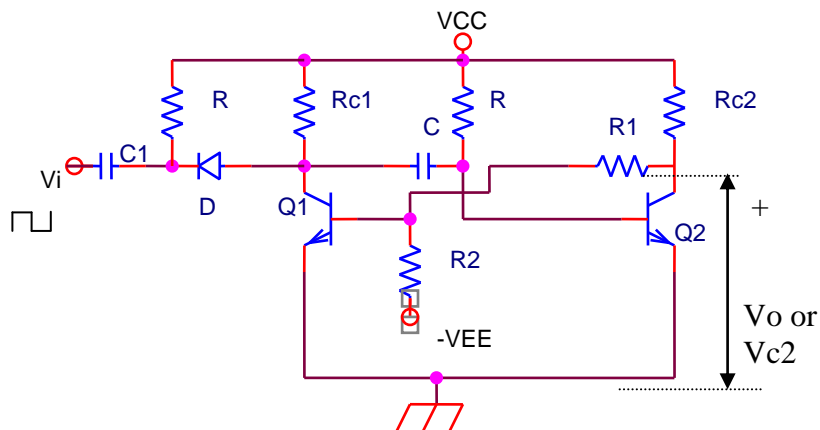

**Fig4.1: Monostable Multivibrator**

**Design:-**

**The stable state:**

1) Q1 is OFF and Q2 is ON

2)  $R_{c2} = V_{CC} - V_{CEsat} / I_c$

$$V_{B1} = -V_{bb} R_1 / (R_1 + R_2) + V_{CEsat} R_2 / (R_1 + R_2) = V_f$$

In order that Q1 be off, we require that  $|V_f| < 0(\text{Si})$  or  $|V_f| < 0.1V(\text{Ge})$

$R = V_{CC} - V_{BESat} / I_{b2}$  when Q2 is in saturation  $I_{b2} \geq I_c / h_{fe}$ .

**The quasi stable state:**

3) Q1 is ON and Q2 is OFF

$$R_{c1} = R_{c2}$$

Assume 10% of  $I_c$  is flowing in  $R_2$

$$I_2 = I_c / 10, V_{r2} = V_{b1} + V_{EE}$$

$$R_2 = V_{r2}/I_2$$

$$I_1 = I_{b1} + I_2$$

When Q2 is OFF


$$R_{c2} + R_1 = V_{ce} - V_{besat}/I_1$$

$$R_1 = V_{cc} - V_{besat}/I_1 - R_{c2}$$

$$T = RC \ln (V_{cc} + I_c R_c - V_{\sigma}) / V_{cc} - V_r$$

$$C = T / (R * \ln (V_{cc} + I_c R_c - V_{\sigma}) / V_{cc} - V_r).$$

**O/P waveforms:-**

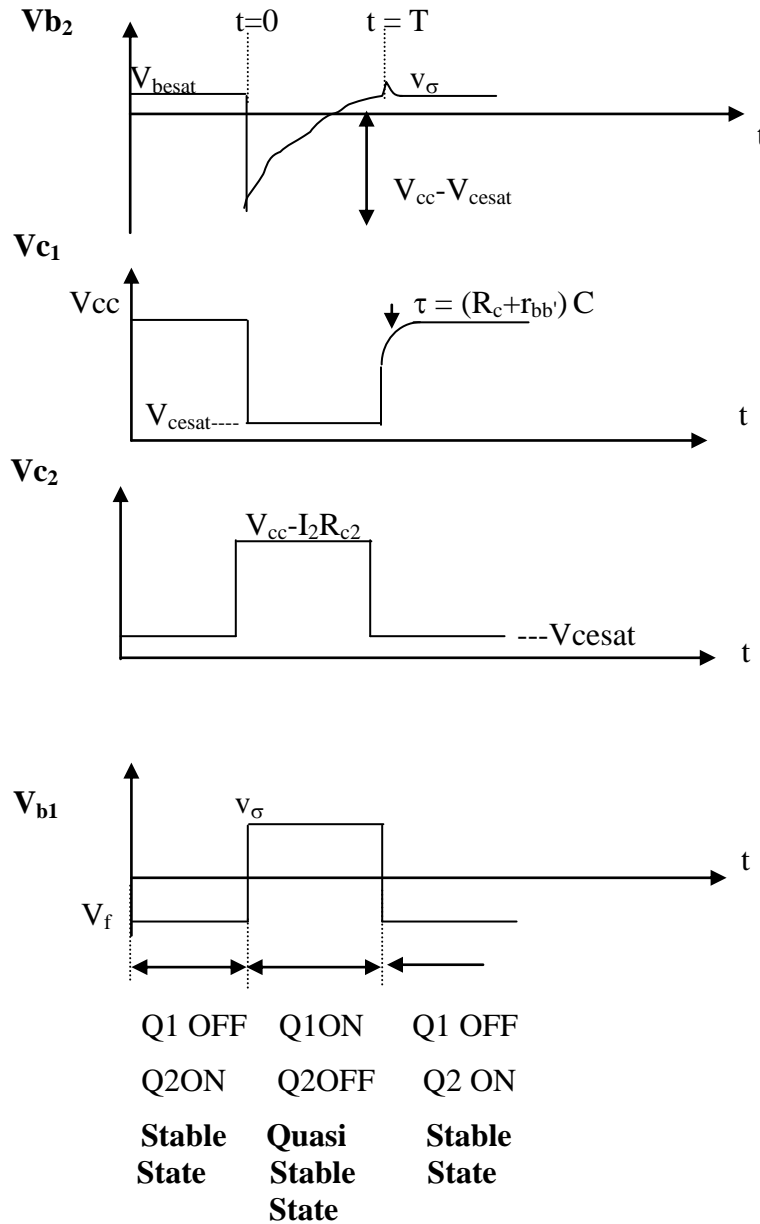

### **Procedure:-**

- Construct the Monostable Multivibrator circuit in fig4.1. using the component values determined in design.
- Measure and record dc voltage levels at the base, emitter and collector terminals of each transistor.
- Add the triggering circuit and apply a square wave input to Cc.
- Observe the waveform at the collector and base of each transistor and record in a form that shows all waveforms time referenced to the input. Also, note the waveform amplitudes and the pulse and space widths.

### **Observations:-**

**Before trigger (i.e.,  $t < 0$ )**

Vc1 = \_\_\_\_\_ V      Vb1 = \_\_\_\_\_ V  
Vc2 = \_\_\_\_\_ V      Vb2 = \_\_\_\_\_ V

**After trigger ( $0 < t < T$ )**

Vc1 = \_\_\_\_\_ V      Vb1 = \_\_\_\_\_ V  
Vc2 = \_\_\_\_\_ V      Vb2 = \_\_\_\_\_ V

**After quasi stable state duration ( $t > T$ )**

Vc1 = \_\_\_\_\_ V      Vb1 = \_\_\_\_\_ V  
Vc2 = \_\_\_\_\_ V      Vb2 = \_\_\_\_\_ V

### **Analysis:-**

- Discuss the dc voltage levels measured throughout the Monostable circuit and compare to the voltage levels in design.
- Explain the waveform obtained from the Monostable circuit and discuss the effect of doubling the capacitor value.

