

12. VOLTAGE REGULATOR USING OP-AMP

AIM:

To design a high current, low voltage and high voltage linear variable dc regulated power supply and test its line and load regulation.

APPARATUS REQUIRED:

S.NO	APPARATUS	SPECIFICATION	QUANTITY
1.	Transistors	TIP122,2N3055	1 each
2.	Integrated Circuit	LM723	1
3.	Digital Ammeter	(0 – 10) A	1
4.	Digital Voltmeter	(0 – 20) V	1
5.	Variable Power Supply	(0 – 30) V-2A	1
6.	Resistors	300 Ω ,430 Ω ,1K Ω ,678K Ω ,67 8 Ω 1 Ω	1 each 2
7.	Capacitors	0.1 μ F,100pF	1 each
8.	Rheostat	(0 – 350) Ω	1

THEORY:

A voltage regulator is an [electrical regulator](#) designed to automatically maintain a constant [voltage](#) level. A voltage regulator may be a simple "feed-forward" design or may include [negative feedback control loops](#). It may use an electromechanical [mechanism](#), or electronic components. Depending on the design, it may be used to regulate one or more [AC](#) or [DC](#) voltages. Load regulation is the change in output voltage for a given change in load current. Line regulation or input regulation is the degree to which output voltage changes with input (supply) voltage changes - as a ratio of output to input change. Active regulators employ at least one active (amplifying) component such as a transistor or operational amplifier. linear regulator is a [voltage regulator](#) based on an active device (such as a [bipolar junction transistor](#), [field effect transistor](#) or [vacuum tube](#)) operating in its "linear region"


PROCEDURE:

Line Regulation:

1. Give the circuit connection as per the circuit diagram
- 2Set the load Resistance to give load current of 0.25A
- 3Vary the input voltage from 7V to 18V and note down the corresponding output voltages
- 4Similarly set the load current (I_L) to 0.5A & 0.9A and make two more sets of measurements.

Load Regulation:

- 1 Set the input voltage to 10V.
- 2 Vary the load resistance in equal steps from 350Ω to 5Ω and note down the corresponding output voltage and load current.
- 3 Similarly set the input voltage (V_{in}) to 14V & 18V and make two more sets of measurements.

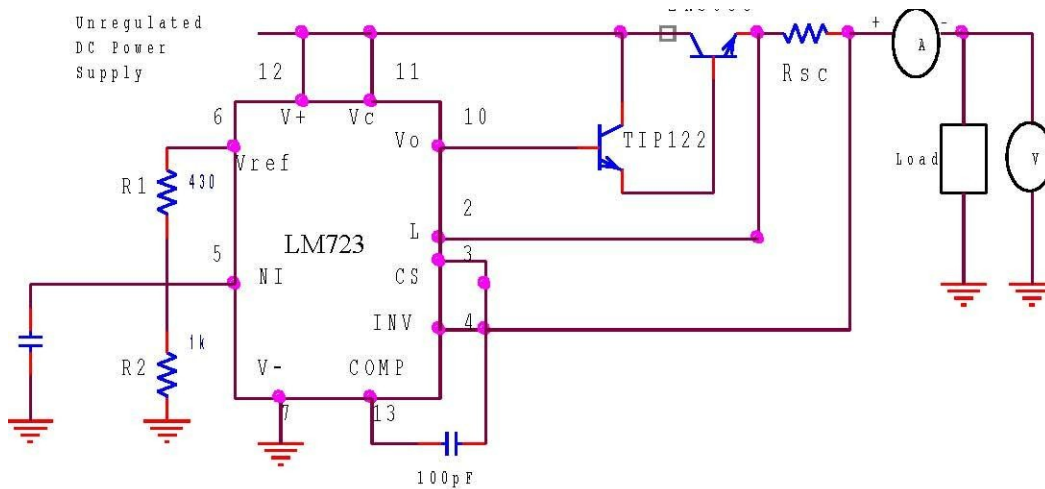CIRCUIT DIAGRAM:**DESIGN:**

$V_o = 5V$, $V_{ref} = 7.15V$

To calculate R_1 , R_2 , R_3 and R_{sc} .

$$V_o = V_{ref} \left(\frac{R_2}{R_1 + R_2} \right)$$

$$5 / 7.15 = \left(\frac{R_2}{R_1 + R_2} \right)$$

$$(R_1 + R_2) 0.699 = R_2$$

$$0.699R_1 = 0.301R_2, R_1 = 0.4306R_2$$

Select **$R_2 = 1K\Omega$**

$$R_1 = 1K\Omega * 0.4306 = 430\Omega$$

$R_1 = 430\Omega$

$$R_3 = R_1 * R_2 / (R_1 + R_2), R_3 = 430.6 * 1000 / (430.6 + 1000)$$

$R_3 = 300\Omega$



$$R_{sc} = V_{sense} / I_{limit} = 0.5 / 1A = 0.5\Omega, R_{sc} = 0.5\Omega$$

Load Regulation:

S.No:	I/P Voltage (V)	O/P Voltage (V)
1)	1	5
2)	2	5
3)	3	5
4)	4	4.7
5)	5	4.7
6)	6	4.6

Line Regulation:

S.No:	I/P Voltage	
	O/P Current (mA)	O/P Voltage (V)
1)	1	1.5
2)	2	2.3
3)	3	3.1
4)	4	4.4
5)	5	4.9
6)	6	5
7)	7	5
8)	8	5

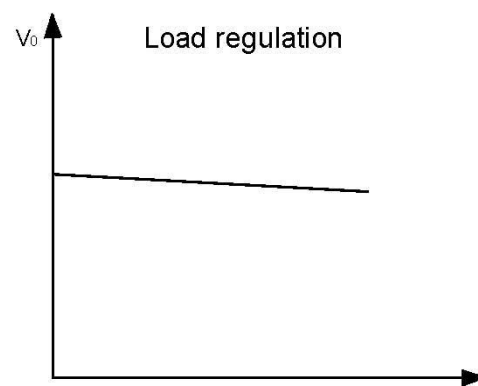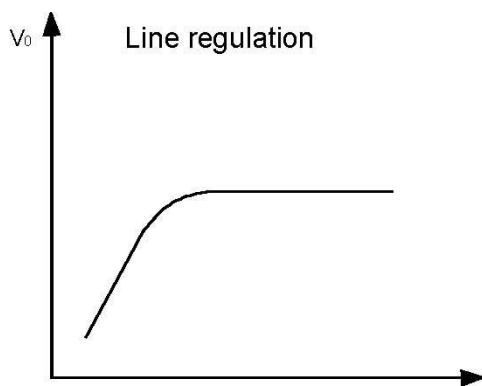

RESULT:

Thus the line and load regulation of low voltage linear variable dc regulated power supply was designed and tested.