

1.Objectives:

1. Understanding the construction and operational principles of digital decoders and encoders.

2.Theory:

✍

Decoders:



A decoder is a logic circuit that will detect the presence of a specific binary number or word. The input to the decoder is a parallel binary number and the output is a binary signal that indicates the presence or absence of that specific number.

It is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines.

• 2-to-4 decoder:


Inputs		Outputs			
B	A	F1	F2	F3	F4
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1
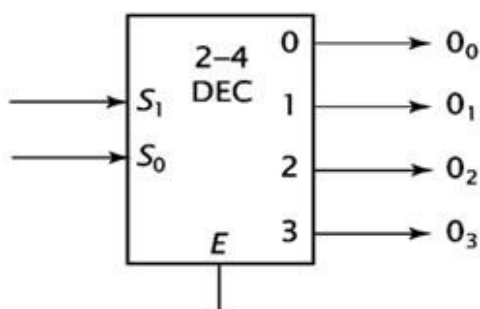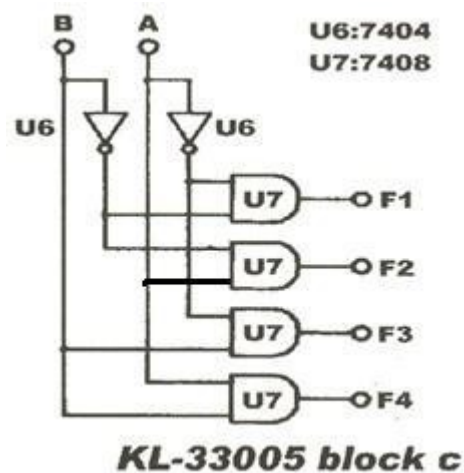
$$\begin{aligned}
 F1 &= A \cdot \bar{B} \\
 F2 &= \bar{A} \cdot B \\
 F3 &= A \cdot B \\
 F4 &= \bar{A} \cdot \bar{B}
 \end{aligned}$$



S_1	S_0	E	O_0	O_1	O_2	O_3
X	X	0	0	0	0	0
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1

3-to-8 decoder:

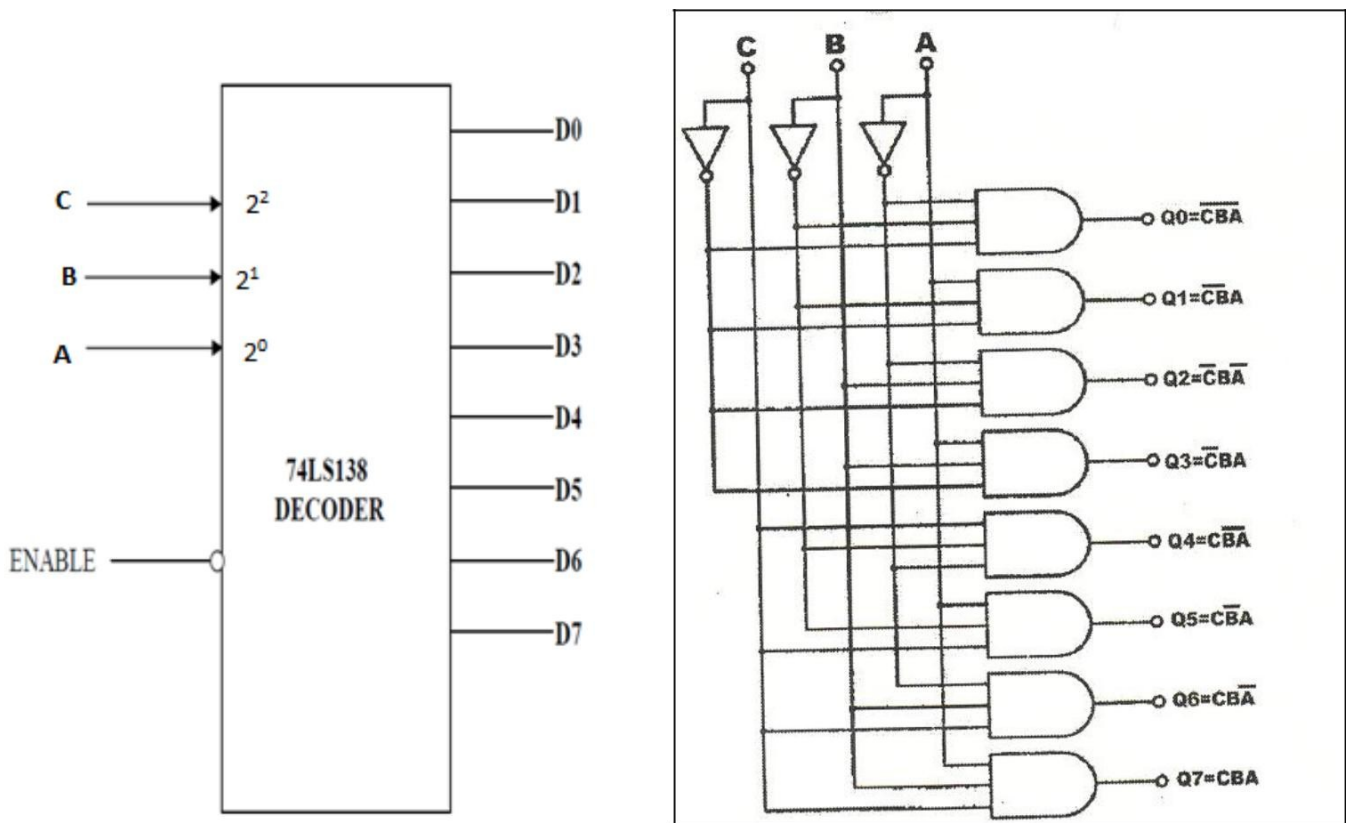


Example:

Implement the following truth table using a decoder and OR gate.

Inputs			Output
A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



Solution:

$$F(A,B,C) = \sum(1,2,4,7)$$

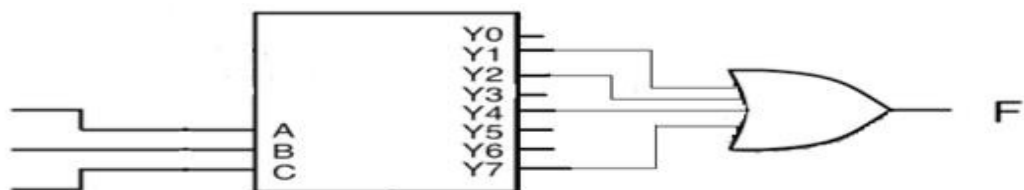

□ **BCD-to-Seven Segment decoder:**

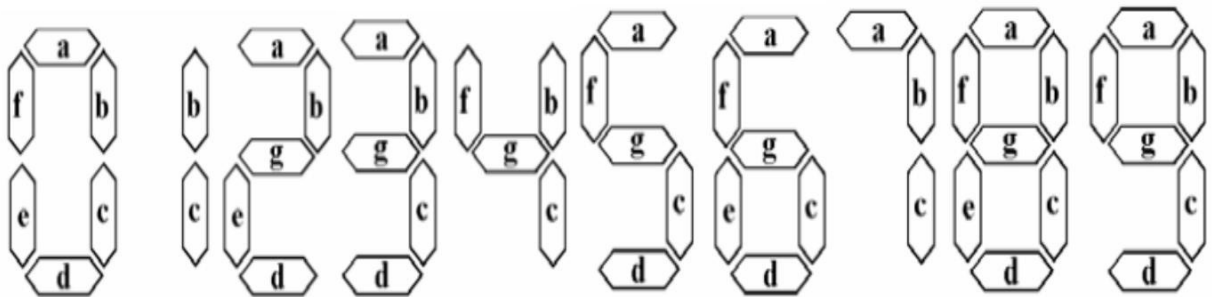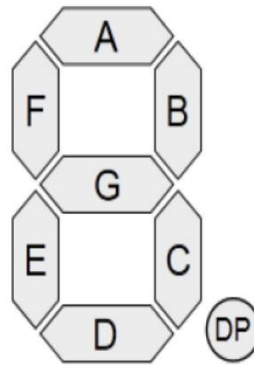A seven segment LED display contains 7 LEDs. Each LED is called a segment and they are identified as (a, b, c, d, e, f, g) segments.



For example if decimal 9 is to be displayed a, b, c, d, f, g must be 0 and the others must be 1 (For common anode type display units), if decimal 5 is to be displayed then a, f, g, c, d must be 0 and the others must be 1.

