

Experiment No.5

ASTABLE MULTIVIBRATOR

Aim:-To design an astable multivibrator to produce a square wave of 5KHz frequency using BC107B.

Components and Equipment:- Resistors, Capacitors, BC107B, RPS, Groove Board and CRO & DMM.

Circuit diagram:-

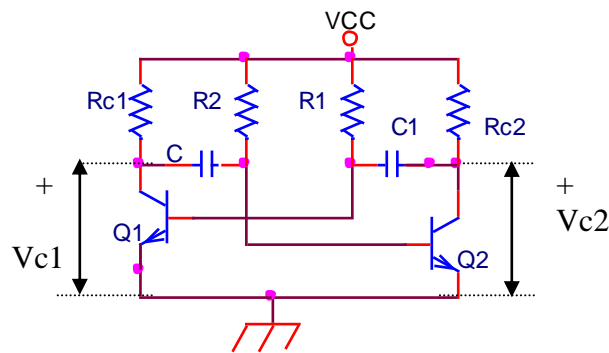


Fig5.1: Astable Multivibrator

Design:-

Given $f = 5\text{KHz}$, V_{cc} , I_{csat} .

$$R_c = (V_{cc} - V_{CESat}) / I_{csat} = 6 - 0.2 / 2\text{mA} = 2.9\text{K}\Omega$$

To ensure saturation

$$I_b > I_{cs} / h_{fe},$$

Hence $R \leq h_{fe} \cdot R_c$

$$R_i = V_{cc} / I_b = 6 / 0.011 = 540\text{K}\Omega.$$

For a symmetrical ckt,

$$R_1 = R_2 = R; C_1 = C_2 = C;$$


$$T/2 = 0.69$$

$$C = T/2 / (0.69RC) = 2.68 \times 10^{-10} \text{ f} = 268 \text{ pf}$$

Procedure:-

- Construct the astable multivibrator circuit in fig5.1 using a 5V supply and the component values determined in design.
- Use an oscilloscope to observe the waveform at the collector and base of each transistor, and record in a form that shows all waveforms time referenced to each other. Also, note the waveform frequency and amplitude.
- Double one of the capacitors by paralleling it with another capacitor. Note the effect on the transistor waveform.

Observations:-

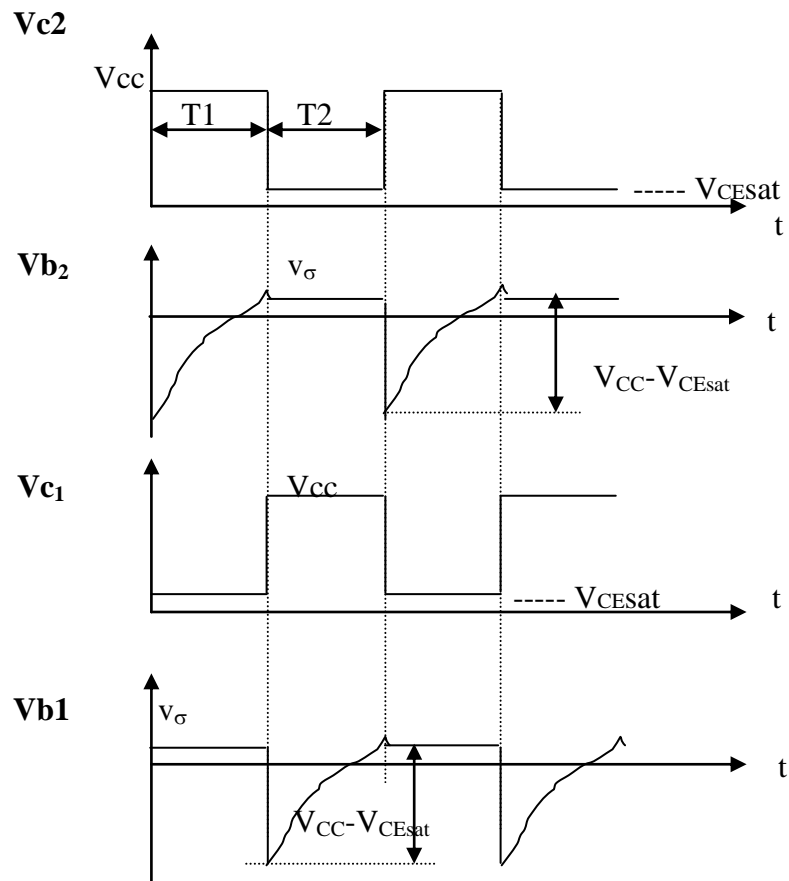

For an asymmetrical circuit,

$$R_1 \neq R_2 \text{ or } C_1 \neq C_2.$$

$$T = T_1 + T_2;$$

$$\text{Where } T_1 = 0.69R_1C_1$$

$$T_2 = 0.69R_2C_2$$

$$T = T_1 + T_2 = 0.69 (R_1C_1 + R_2C_2)$$

Analysis:-

- Explain the waveforms obtained from the Astable circuit and compare the amplitudes and frequency to the design values (in example).
- Discuss the effect of doubling the capacitor value.

Conclusion:-

Without the aid of the external triggering circuit, the astable configuration makes transition from one quasi-stable state into another.